

## Discussion Questions

1 How many gates does your one-bit multiplexer use? The 32-bit multiplexer? Write down a formula for an N-bit multiplexer.

one-bit multiplexer uses 4 gates.

32-bit multiplexer uses 128 gates.

N-bit multiplexer uses  $n \cdot 4$  gates.

2 We wrote a polymorphic function implementing an N-bit multiplexer. Explain how to write a polymorphic version of the left shifter.


Because left shifting involves adding zeros to the end of the data, we can remove the flag checks. Modify the calculation of the result as follows:

```
result = multiplexerN(shamt[0], operand, {operand[30:0], bitProvider(1'b0, 1)});
result = multiplexerN(shamt[1], result, {operand[29:0], bitProvider(1'b0, 2)});
...
```

3 One purpose of this lab was to demonstrate a microarchitectural optimization. How many gates did we save by combining the logical and arithmetic right shifts?

Implementing it separately requires 10 MUXes, while implementing it together requires 5 MUXes. Therefore, we save 5 MUXes, which amounts to 640 gates ( $5 \cdot 32 \cdot 4$ ).

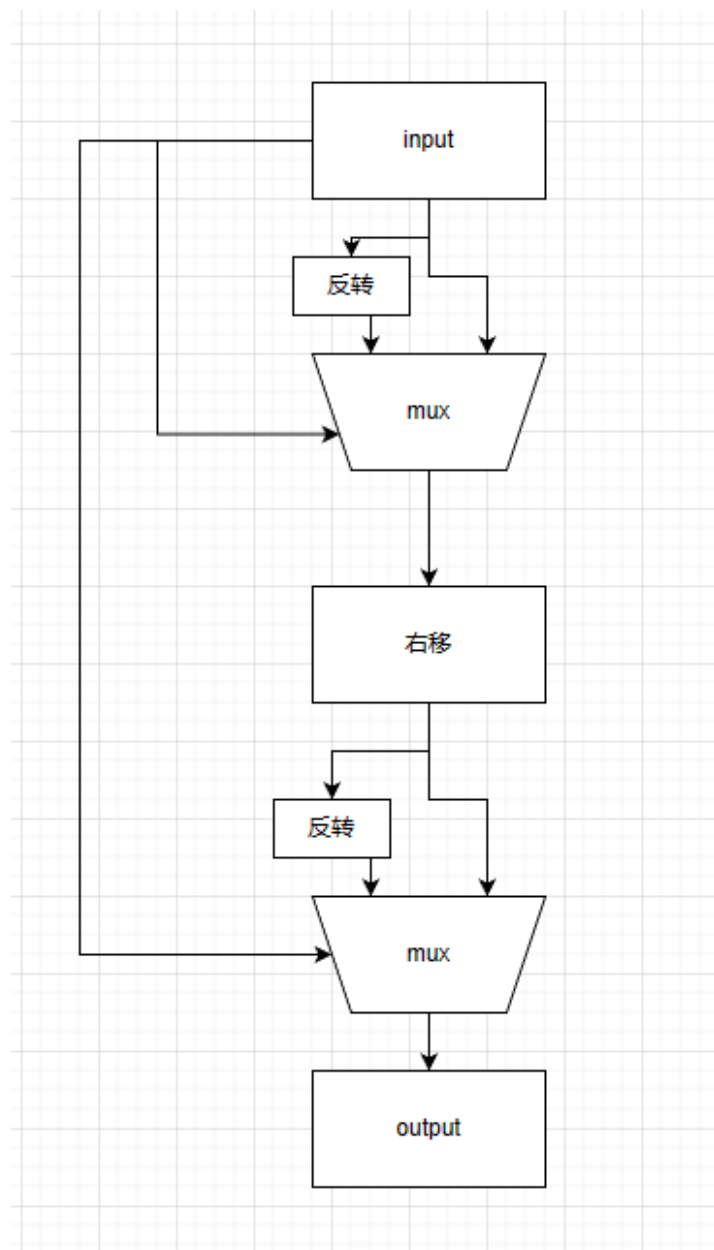4 Our right shifter handles right shifts only. However, with a small extension, it can handle left shifts as well. Draw a microarchitecture for this kind of combined shifter. How much hardware do we save?



Combining the left shifter saves 5 MUXes, and combining the arithmetic right shifter and logical right shifter saves another 5 MUXes. In total, we save 10 MUXes, which amounts to 1280 gates ( $10 * 32 * 4$ ).